

Roll No. _____

25/1658**B.C.A. (Second Semester)****Examination, 2025****Paper : Second****Digital Electronics & Computer****Organization***Time : Two Hours / [Maximum Marks : 75***Note :** Attempt **all** sections as per instructions.**Section-A****(Very Short Answer Type Questions)**

Note : Attempt all **5 (five)** questions. Each question carries **2(two)** marks and the answer of each question should not exceed 50 words. $5 \times 2 = 10$

1. (i) What is cache memory? Explain
- (ii) What is Associate memory.

P.T.O.**25/1658**

- (iii) Binary code and BCD code.
- (iv) What is SOP and POS?
- (v) What is Universal Gate?

Section-B**(Short Answer Type Questions)**

Note : Attempt any **5 (five)** question out of total **8 (eight)** question. Each question carries **5 (five)** marks and answer of each question should not exceed 100 words. $5 \times 5 = 25$

2. (i) Describe the mode of working of an edge triggered S-R flip flop.
- (ii) What are "Don't care conditions"? Discuss how they are handled, with the help of an example.
- (iii) Draw the Truth Table and the symbol for the following gates:
 - (a) XNOR
 - (b) NAND
 - (c) XOR

- (iv) Describe the working of full adder with the help of clear circuit diagram and truth table.
- (v) Explain with formula, the De Morgan's Laws. Prove them with the help of truth table.
- (vi) Describe and discuss the operation of a T-type Flip flop.
- (vii) Minimize the given Boolean function using K-maps and implement the simplified function using NAND gates only.

$$F(A, B, C, D) = m(0, 1, 2, 9, 11, 15) + d(8, 10, 14).$$
- (viii) How is a RAM constructed? Discuss the different technology used in constructing the RAM of a computer, with their relative advantages and disadvantages.

Section-C

(Long Answer Type Questions)

Note : Attempt any **2 (two)** out of **4 (four)** questions. Each question carries **20 (twenty)** marks and the answer of each question should not exceed **400 words**.

2 × 20 = 40
P.T.O.

3. (i) What do you understand by virtual memory? Explain the basic organization and working methodology of virtual memory.
- (ii) Explain briefly:
 - (a) Race Around condition and its solution
 - (b) D Flip Flop using NAND gates
- (iii) Distinguish between:
 - (a) Combinational and sequential Circuits
 - (b) Synchronous and Asynchronous counter
 - (c) T flip flop and D flip flop
- (iv) Using the postulates of Boolean Algebra, simplify the following expression.
 - (a) $AB + A(B + C) + B(B + C)$
 - (b) $AB(C + BD) + AB$
 - (c) $ABC + (A + B + C)ABCD$
 - (d) $AB + ABC + BCD + BE$